

Problem Domain:

A combinational circuit is used to control a seven-segment display of decimal digits, as shown in Figure 20.36. The circuit has four inputs, which provide the four-bit code used in binary representation. The seven outputs define which segments will be activated to display a given decimal digit.

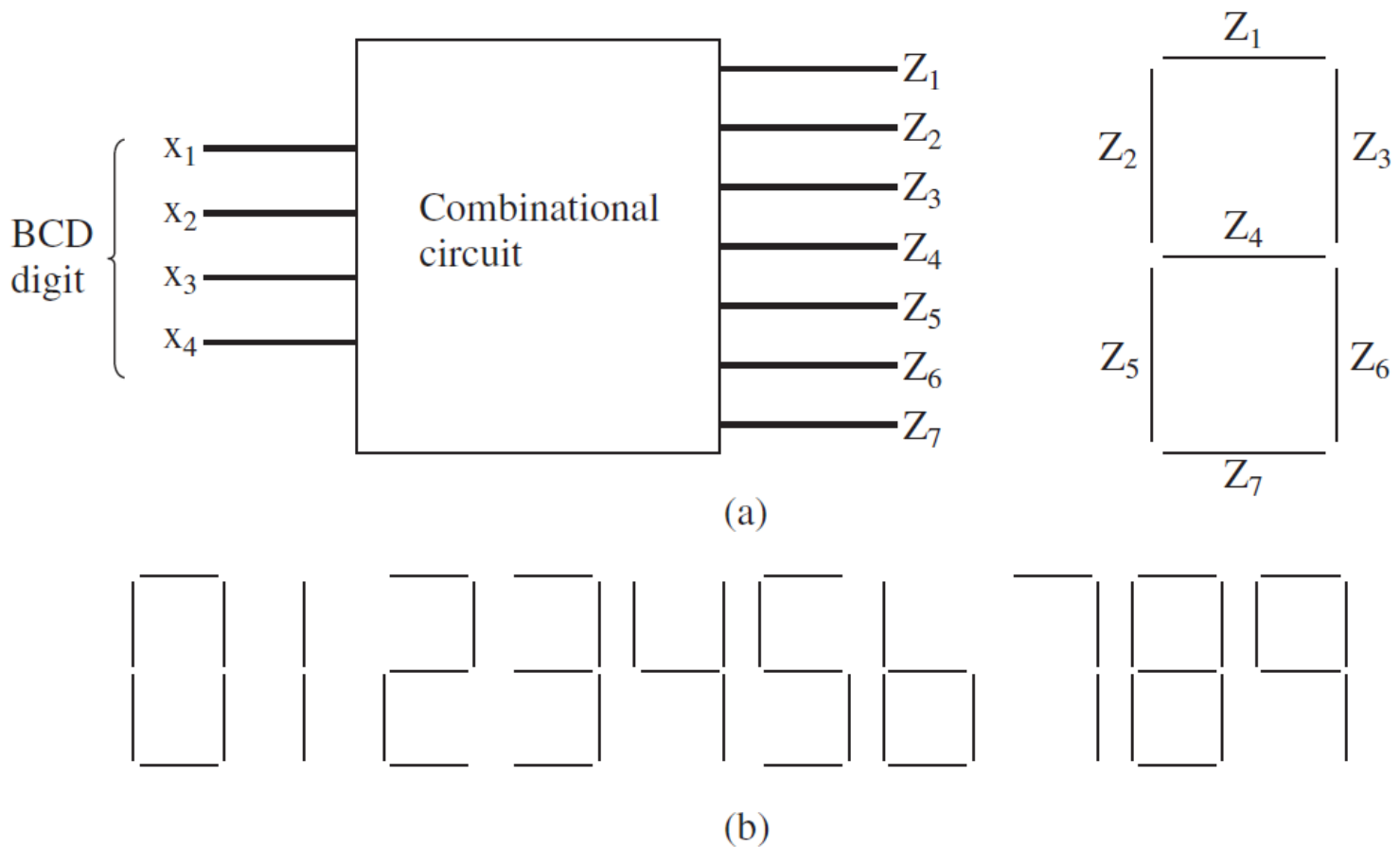


Figure 20.36 Seven-Segment LED Display Example

We have provided the template for the 'TRUTH TABLE' (LAB7-2-table) that simulates the combinatorial circuit described above.

TO DO: Complete the provided LAB7-2-table doc:

- 1) the TRUTH TABLE and
- 2) Express Z_1 to Z_7 in SOP form.

DELIVERABLES:

Upload the completed work.