
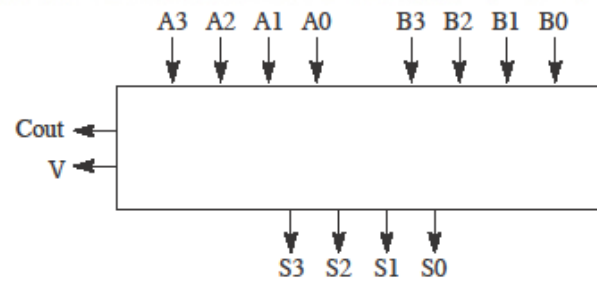


You may choose to use free hand drawing in answering the questions and then ‘scanning’ and submitting as a .jpeg or .pdf

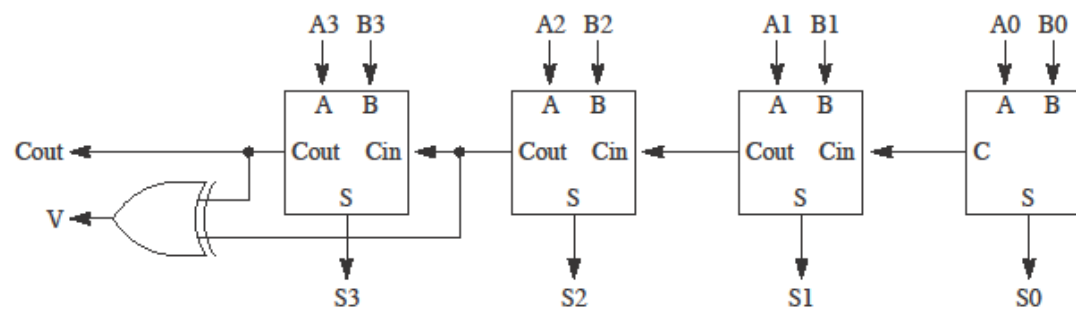
- 1) The eXclusive NOR gate, written XNOR, is equivalent to an XOR followed by an inverter.
 - a) Draw the logic symbol for a two input XNOR gate.
 - b) Construct its truth table.
 - c) The XNOR is also called a ‘comparator’, WHY?
- 2) Identify each gate in Fig. 10.63(attached), as one of the following:
 - 1) an AND gate, 2) an OR gate, 3) a NAND gate, 4) a NOR gateIndicate it as: a=?, b=?.....
- 3) Write the Boolean expressions for the logic diagrams in Fig 10.62(attached)
- 4) Modify Fig 10.52(b)(attached) to provide two additional outputs, one for the ‘N’ bit and one for the ‘Z’ bit.
- 5) Implement the following logical units (LU’s) for the PEP/8 ALU: use Fig. 10.59(attached) as a guideline
 - a) LU5, A **AND** B
 - b) LU7, A **OR** B
 - c) LU9, A **XOR** B




(a) Block diagram.




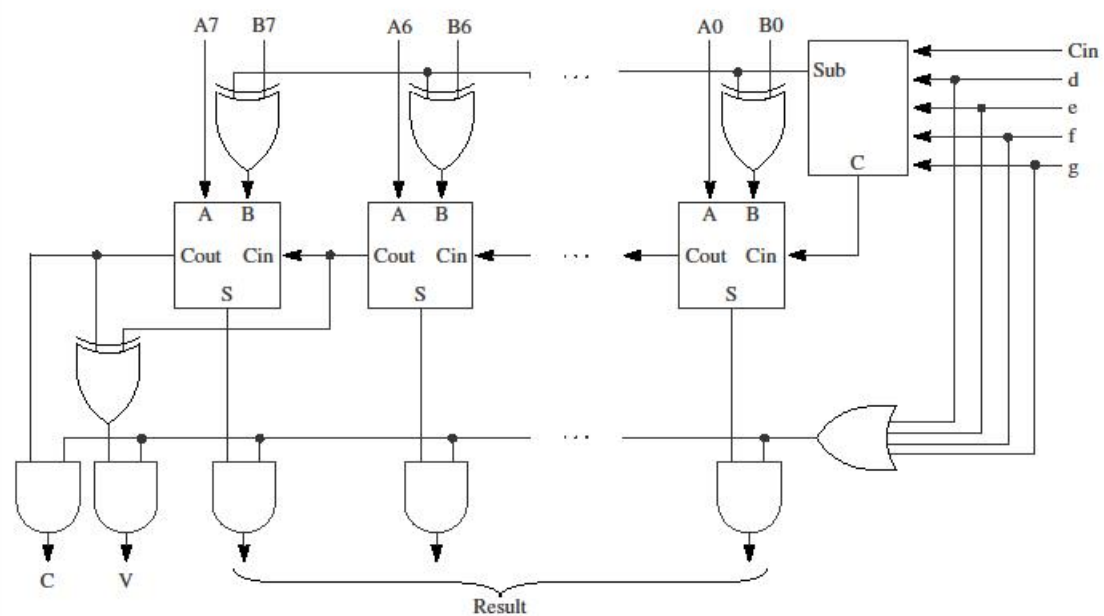(b) Implementation. © 2013 Jones and Bartlett Publishers, LLC (www.jbpubs.com)




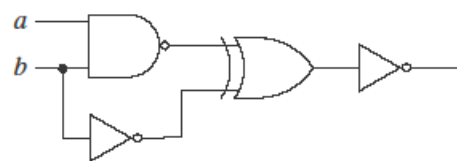

(a)

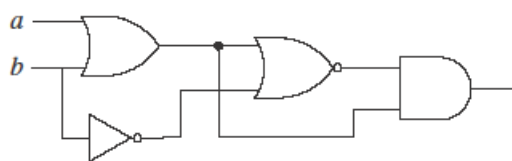

(b)

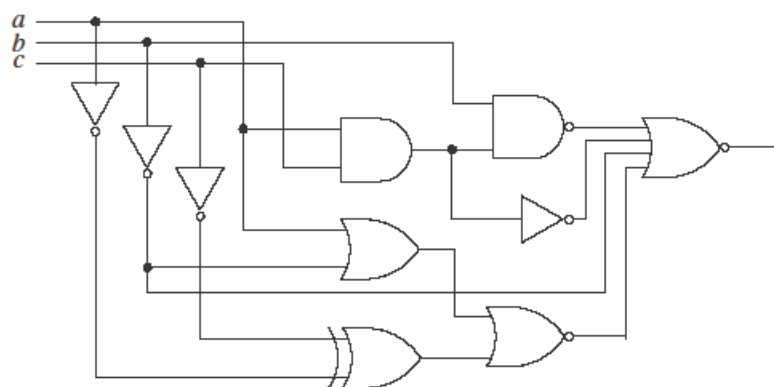

(c)

